

# **ECE3201**

**HW #3 due September 15, 2014**

## **Electronic Circuit Design and Analysis**

Chapter 2 problems:

Use Approximate Equivalent Model for

2.33, 2.36, 2.39, 2.43, 2.45, 2.47

Use Ideal Diode model for 2.31

Book: Electronic Devices and Circuit Theory  
by Robert L Boylestad and Louis Nashelsky; Eleventh Edition