

## ECE 249 Lab 3

Spring 2005

The figure below shows the schematic diagram for a NAND gate with  $W_n = W_p = 2\mu\text{m}$ , and  $L$  for both NMOS and PMOS =  $0.6\mu\text{m}$ .

- (i) Draw the schematic for this circuit on Cadence.
- (ii) Make a symbol for this circuit.
- (iii) To test your circuit, plot the input output characteristics.

 


Fig. 1 Schematic diagram of a NAND gate.

### **HAND IN**

1. Schematic for the above NAND gate
2. Input/output waveform showing all possible inputs for A & B
3. What is the worst-case propagation delay and on what input line?.