 


Topics

- Performance Characterization
 - Interconnect Delay
 - Gate Delay
 - Switching Characteristics

Interconnect delay



- Charge V_{in} to V_{DD}


- The transient output voltage is $V_{out}(t) = V_{DD} \left(1 - e^{-\frac{t}{RC}} \right)$

$$\frac{V_{DD}}{2} = V_{DD} \left(1 - e^{-\frac{t_{dlh}}{RC}} \right)$$

$$\frac{t_{dlh}}{RC} = -\ln\left(\frac{1}{2}\right)$$

$$t_{dlh} \approx .69RC$$


Interconnect delay

 

- More accurate than lumped RC model
- More difficult to solve for large N
- Need full-scale SPICE simulation

Elmore Delay

 
- Single line model not useful for generalized RC tree networks



Elmore Delay

- First order calculation of time constant of the circuit
 
$$t_d = \sum_{j=1}^N C_j \sum_{k \in \text{path}} R_k$$



$$t_{d3} = R_1 C_1 + (R_1 + R_2) C_2 + (R_1 + R_2 + R_3) C_3 + R_1 C_4$$


$$t_{d4} = R_1 C_1 + R_1 C_2 + R_1 C_3 + (R_1 + R_4) C_4$$

Elmore Delay


$$t_d = \sum_{j=1}^N C_j \sum_{k \in \text{path}} R_k$$

$$t_{d3} = R_1(C_1 + C_2 + C_3 + C_4) + R_2(C_2 + C_3) + R_3C_3$$
 
$$t_{d4} = R_1(C_1 + C_2 + C_3 + C_4) + R_4C_4$$



Elmore Delay

 


$$t_d = \sum_{j=1}^N \frac{C}{N} \sum_{k=1}^j \frac{R}{N}$$
$$= \frac{C}{N} \frac{R}{N} \frac{N(N+1)}{2} = RC \left(\frac{N+1}{2N} \right)$$

$$t_d = \frac{RC}{2} \text{ for } N \rightarrow \infty$$


Interconnect Delay
 
$$\begin{aligned}t_d &= 8\Omega(20\text{ fF} + 10\text{ fF}) + 4\Omega(10\text{ fF}) \\ &= .28\text{ ps}\end{aligned}$$



Interconnect Delay

 
$$t_d = 8\Omega(20\text{ fF} + 10\text{ fF} + 10\text{ fF} + 10\text{ fF}) + 4\Omega(10\text{ fF})$$
$$= .44\text{ ps}$$



Interconnect Delay

- Fanout Effects
 - Lines with multiple loads will have longer delays
 - Clocks
 - Data buses
 - Control lines
 - Solutions
 - Wider and thicker lines for special signals
 - Buffer drivers

Interconnect Delay

 

$$t_d = \sum_{j=1}^N \frac{C}{N} \sum_{k=1}^j \frac{R}{N}$$
$$= \frac{C}{N} \frac{R}{N} \frac{N(N+1)}{2} = RC \left(\frac{N+1}{2N} \right)$$


$$t_d = \frac{RC}{2} \text{ for } N \rightarrow \infty$$

Interconnect Delay

$$\begin{aligned}t_d &= \frac{RC}{2} \\ &= \frac{1}{2} \left(r \frac{l}{w} \right) (c_a lw + c_p (l + w)) \\ &\approx \frac{1}{2} r c_a l^2\end{aligned}$$

- Delay is proportional to the square of the length
- Try to avoid long lines

Interconnect Delay

 

- Interconnect resistance

$$R = .07 \frac{5000\mu}{0.5\mu} = 700\Omega$$

- Interconnect capacitance

$$C_{wire} = .03 \cdot 5000\mu \cdot 0.5\mu + .044 \cdot 2 \cdot (5000\mu + 0.5\mu) = 515 fF$$

- Intrinsic load capacitance


$$C_{in} \approx 5 fF$$

- Propagation delay

$$t_p = \frac{RC_{wire}}{2} + RC_{in} = \frac{700 \cdot 515 fF}{2} + 700 \cdot 5 fF = 184 ps$$

Interconnect Delay

 - Avoid long interconnect delays using buffers



- Interconnect resistance

$$R = .07 \frac{2500\mu}{0.5\mu} = 350\Omega$$

- Interconnect capacitance

$$C_{wire} = .03 \cdot 2500\mu \cdot 0.5\mu + .044 \cdot 2 \cdot (2500\mu + 0.5\mu) = 258 fF$$

- Intrinsic load capacitance


$$C_{in} \approx 5 fF$$

- Propagation delay

$$t_p = 2 \cdot \left(\frac{RC_{wire}}{2} + RC_{in} \right) = 2 \cdot \left(\frac{350 \cdot 258 fF}{2} + 350 \cdot 5 fF \right) = 94 ps$$

Interconnect Delay

 - Avoid long interconnect delays using wider lines



- Interconnect resistance

$$R = .07 \frac{5000\mu}{5\mu} = 70\Omega$$

- Interconnect capacitance

$$C_{wire} = .03 \cdot 5000\mu \cdot 5\mu + .044 \cdot 2 \cdot (5000\mu + 5\mu) = 1190 fF$$

- Intrinsic load capacitance

$$C_{in} \approx 5 fF$$

- Propagation delay


$$t_p = \frac{RC_{wire}}{2} + RC_{in} = \frac{70 \cdot 1190 fF}{2} + 70 \cdot 5 fF = 42 ps$$

Interconnect delay

- Interconnect sizing
 - Adjust delays
 - Prevent metal migration
 - Power supply noise and signal integrity


Interconnect Delay

- Directional Behavior

 


$$R_s = .08 \Omega/\square$$

$$C_a = .02 \text{ fF}/\mu^2$$

 

$$t_d = 2\Omega(20 \text{ fF} + 10 \text{ fF}) + 4\Omega(10 \text{ fF})$$

$$= .10 \text{ ps}$$

 


$$t_d = 4\Omega(10 \text{ fF} + 20 \text{ fF}) + 2\Omega(20 \text{ fF})$$

$$= .16 \text{ ps}$$

Switching Delay



- The intrinsic delay of a gate
- Transistor sizing can affect the delay
- Extrinsic capacitances can affect the delay

Delay Definitions

 

Switching Delay

- Fall time analysis

  

Fall time analysis

- Saturated Mode

$$I_C = I_{DS}$$

$$-C_L \frac{dV_{out}}{dt} = k_n \frac{(V_{DD} - V_{tn})^2}{2}$$

$$dt = -2 \frac{C_L}{k_n (V_{DD} - V_{tn})^2} dV_{out}$$

$$t_{f1} = 2 \frac{C_L}{k_n (V_{DD} - V_{tn})^2} \int_{V_{DD} - V_m}^{.9V_{DD}} dV_{out}$$

$$t_{f1} = 2 \frac{C_L (V_{tn} - .1V_{DD})}{k_n (V_{DD} - V_{tn})^2}$$

Fall time analysis

- Linear Mode

$$I_C = I_{DS}$$

$$-C_L \frac{dV_{out}}{dt} = k_n \left[(V_{DD} - V_{tn})V_{out} - \frac{V_{out}^2}{2} \right]$$

$$dt = \frac{-2C_L}{k_n (2(V_{DD} - V_{tn})V_{out} - V_{out}^2)} dV_{out}$$

$$t_{f2} = \frac{-2C_L}{k_n} \int_{.1V_{DD}}^{V_{DD} - V_{tn}} \frac{dV_{out}}{(2V_{out}(V_{DD} - V_{tn}) - V_{out}^2)}$$

Fall time analysis

- Linear Mode

$$\begin{aligned} t_{f2} &= \frac{C_L}{k_n(V_{DD} - V_{tn})} \ln \left(\frac{V_{out}}{2(V_{DD} - V_{tn}) - V_{out}} \right) \Bigg|_{.1V_{DD}}^{V_{DD} - V_{tn}} \\ &= \frac{C_L}{k_n(V_{DD} - V_{tn})} \ln \left(\frac{19V_{DD} - 20V_{tn}}{V_{DD}} \right) \end{aligned}$$

Fall time analysis

$$\begin{aligned}t_f &= t_{f1} + t_{f2} \\&= \frac{C_L}{k_n(V_{DD} - V_{tn})} \left(\frac{2(V_{tn} - .1V_{DD})}{V_{DD} - V_{tn}} + \ln \left(\frac{19V_{DD} - 20V_{tn}}{V_{DD}} \right) \right) \\&= \frac{C_L}{k_n V_{DD} (1 - n)} \left(\frac{2(n - .1)}{1 - n} + \ln(19 - 20n) \right) \quad n = \frac{V_{tn}}{V_{DD}} \\K &= \frac{1}{(1 - n)} \left(\frac{2(n - .1)}{1 - n} + \ln(19 - 20n) \right) \\t_f &= K \frac{C_L}{k_n V_{DD}}\end{aligned}$$

Fall time analysis

- Fall time is proportional to load capacitance and inversely proportional to V_{DD} and k_n
- Decreasing the supply voltage will increase the fall time
- Increasing the transistor width will increase k which will reduce the fall time
- Changing these three parameters can cause conflicting goals

Rise time analysis

$$t_r = \frac{C_L}{k_p V_{DD} (1-p)} \left(\frac{2(p-.1)}{1-p} + \ln(19-20p) \right)$$
$$K_p = \frac{1}{(1-p)} \left(\frac{2(p-.1)}{1-p} + \ln(19-20p) \right) \quad p = \frac{-V_{tp}}{V_{DD}}$$
$$t_r = K_p \frac{C_L}{k_p V_{DD}}$$

Rise time analysis

- For equal fall times and rise times

$$t_f = t_r$$

$$K_n \frac{C_L}{k_n V_{DD}} = K_p \frac{C_L}{k_p V_{DD}}$$


$$k_n = k_p$$

$$\mu_n C_{ox} \left(\frac{W_n}{L} \right) = \mu_p C_{ox} \left(\frac{W_p}{L} \right)$$


$$\frac{W_p}{W_n} = \frac{\mu_n}{\mu_p} \approx 2 - 3$$

Propagation Delay

 - As with interconnect delay, find the equivalent resistance and load capacitance of the transistor



$$t_{pHL} = .69R_{eq}C_L$$

 

Propagation Delay

$$R_{eq} = \text{average}(R_{on}(t)) = \frac{1}{t_2 - t_1} \int_{t_1}^{t_2} \frac{V_{DS}(t)}{I_{DS}(t)} dt$$

- Propagation delay is the time for voltage to reach half way point - so integrate from V_{DD} to $V_{DD}/2$

$$R_{eq} = \frac{1}{V_{DD}/2 - V_{DD}} \int_{V_{DD}}^{V_{DD}/2} \frac{V_{DS}(t)}{I_{DS}(t)} dV_{DS}$$

- For the output range we are interested in, the transistor is always in saturation


$$R_{eq} = \frac{-2}{V_{DD}} \int_{V_{DD}}^{V_{DD}/2} \frac{V_{DS}}{I_{DSAT}(1 + \lambda V_{DS})} dV_{DS}$$

Propagation Delay

$$\begin{aligned}R_{eq} &= \frac{-2}{V_{DD}} \int_{V_{DD}/2}^{V_{DD}/2} \frac{V_{DS}}{I_{DSAT}(1 + \lambda V_{DS})} dV_{DS} \\&= \frac{2}{V_{DD} \lambda^2 I_{DSAT}} \left(\lambda V_{DS} - \ln(1 + \lambda V_{DS}) \right) \Bigg|_{V_{DD}/2}^{V_{DD}} \\&= \frac{2}{V_{DD} \lambda^2 I_{DSAT}} \left(\lambda V_{DS} - \left(\lambda V_{DS} - \frac{\lambda^2 V_{DS}^2}{2} + \frac{\lambda^3 V_{DS}^3}{3} - \dots \right) \right) \Bigg|_{V_{DD}/2}^{V_{DD}} \\&= \frac{2}{V_{DD} I_{DSAT}} \left(\frac{V_{DS}^2}{2} - \frac{\lambda V_{DS}^3}{3} + \dots \right) \Bigg|_{V_{DD}/2}^{V_{DD}} \\&= \frac{2}{V_{DD} I_{DSAT}} \left(\frac{3V_{DD}^2}{8} - \frac{7\lambda V_{DD}^3}{24} + \dots \right) \\&\approx \frac{3}{4} \frac{V_{DD}}{I_{DSAT}} \left(1 - \frac{7}{9} \lambda V_{DD} \right)\end{aligned}$$


Propagation Delay

- Load capacitance

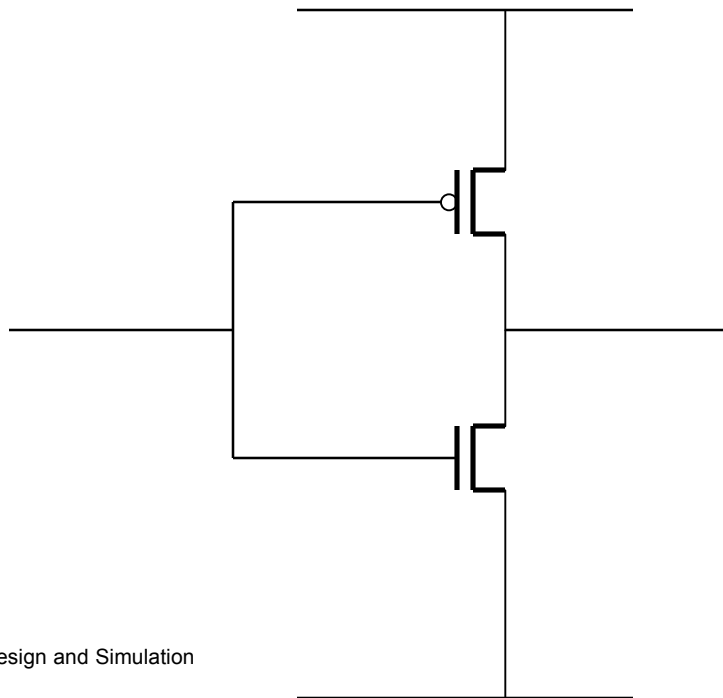

Propagation Delay

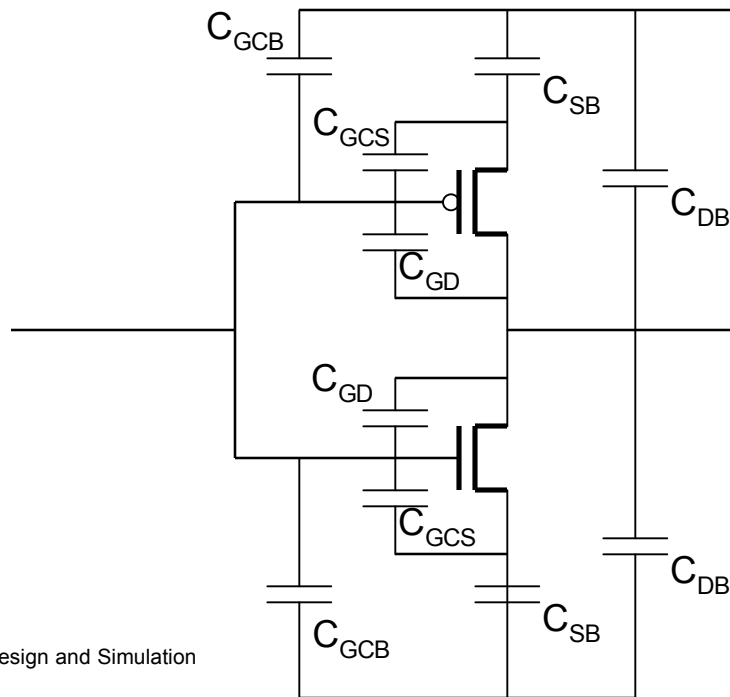- Load capacitance
 - Intrinsic capacitance - sum of capacitances at drain - $C_{GD} + C_{DB}$



Propagation Delay

- Intrinsic Capacitance
 - C_{GD} is composed solely of overlap capacitance
 - The transistors are either in cutoff or in saturation, so no channel capacitance exists
 - The actual load capacitance relative to ground is $2C_{GDO}$ because of Miller effect

Propagation Delay

$$t_{pLH} = 0.69R_{eq} \left(2C_{GDO_n} + 2C_{GDO_p} + C_{DB_n} + C_{DB_p} + C_{ext} \right)$$

- Extrinsic capacitance is composed of wire capacitance and input capacitance of fanout
- Input capacitance is composed of overlap capacitance and channel capacitance
 - Overlap capacitance is $C_{GDO} + C_{GSO}$. Miller effect is ignored because V_{out} is assumed to be constant
 - Channel capacitance is $C_{ox}WL$. Assume worst case
- All capacitances are roughly proportional to W
- Equivalent resistance is inversely proportional to W

Next class

- Delay Analysis
- CMOS Logic Design
- Chapter 6.1 and 6.2