

# Topics


- Dynamic CMOS
- Sequential Design
- Memory and Control

# Dynamic CMOS

- In **static** circuits at every point in time (except when switching) the output is connected to either GND or  $V_{DD}$  via a low resistance path.
  - fan-in of  $n$  requires  $2n$  ( $n$  N-type +  $n$  P-type) devices
- **Dynamic** circuits rely on the temporary storage of signal values on the capacitance of high impedance nodes.
  - requires only  $n+2$  ( $n+1$  N-type + 1 P-type) transistors

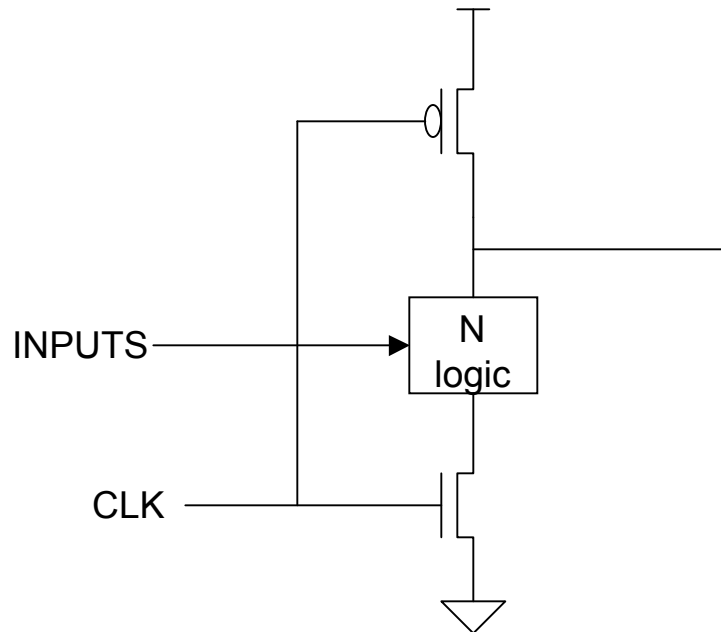
# Dynamic CMOS

- nMOS logic structure with precharged pullup




- Precharge to VDD when clock is low
- Evaluate when clock is high

# Dynamic Gate

 

Two phase operation

Precharge (Clk = 0)  
Evaluate (Clk = 1)

 

# Conditions on Output

- Once the output of a dynamic gate is discharged, it cannot be charged again until the next precharge operation.
- Inputs to the gate can make **at most** one transition during evaluation.
- Output can be in the high impedance state during and after evaluation (PDN off), state is stored on  $C_L$

# Properties of Dynamic Gates

- Logic function is implemented by the PDN only
  - number of transistors is  $N + 2$  (versus  $2N$  for static complementary CMOS)
- Full swing outputs ( $V_{OL} = \text{GND}$  and  $V_{OH} = V_{DD}$ )
- Non-ratioed - sizing of the devices does not affect the logic levels
- Faster switching speeds
  - reduced load capacitance due to lower input capacitance ( $C_{in}$ )
  - reduced load capacitance due to smaller output loading ( $C_{out}$ )
  - no  $I_{sc}$ , so all the current provided by PDN goes into discharging  $C_L$

# Properties of Dynamic Gates


- Overall power dissipation usually higher than static CMOS
  - no static current path ever exists between  $V_{DD}$  and GND (including  $P_{sc}$ )
  - no glitching
  - higher transition probabilities
  - extra load on Clk
- PDN starts to work as soon as the input signals exceed  $V_{Tn}$ , so  $V_M$ ,  $V_{IH}$  and  $V_{IL}$  equal to  $V_{Tn}$ 
  - low noise margin ( $NM_L$ )
- Needs a precharge/evaluate clock

# Dynamic CMOS


- Advantages
  - Fewer transistors than CMOS - on the same order as pseudo-nMOS
  - Smaller load capacitances - faster speed
- Disadvantages
  - Inputs must be stable during evaluate phase
  - Can not be cascaded
  - Charge sharing


 
# Issues in Dynamic Design 1: Charge Leakage




Leakage sources

 


*Dominant component is subthreshold current*

# Solution to Charge Leakage

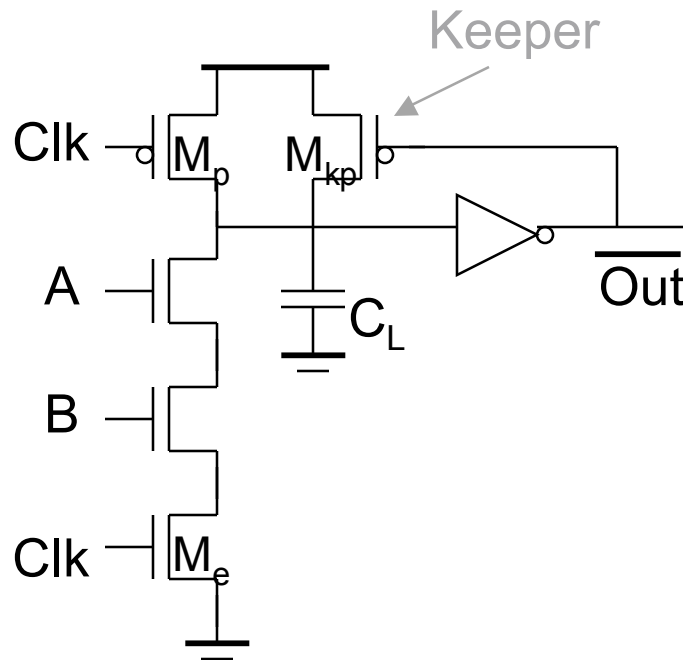

- Same approach as level restorer for pass-transistor logic
- Increase size of inverter to increase capacitance

 
# Issues in Dynamic Design 2: Charge Sharing



Charge stored originally on  $C_L$  is redistributed (shared) over  $C_L$  and  $C_A$  leading to reduced robustness


# Dynamic CMOS

- Charge Sharing

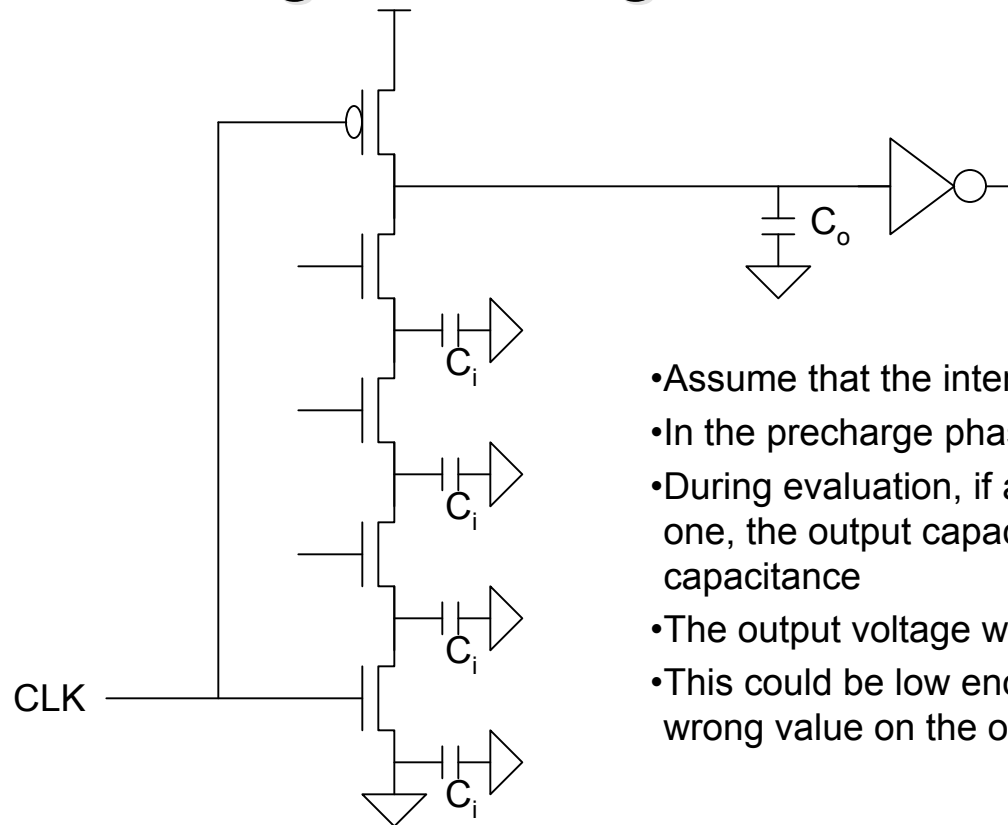

- Assume that the internal capacitances have been discharged
- In the precharge phase, the output capacitance gets charged
- During evaluation, if all the inputs are high except the bottom one, the output capacitance gets distributed to the internal capacitance
- The output voltage will drop to  $V_{DD} \frac{C_o}{C_o + 2C_i}$
- This could be low enough to trigger the inverter, causing a wrong value on the output


# Solution to Charge Redistribution

 

Precharge internal nodes using a clock-driven transistor  
(at the cost of increased area and power)


# Dynamic CMOS

- Cascade problem

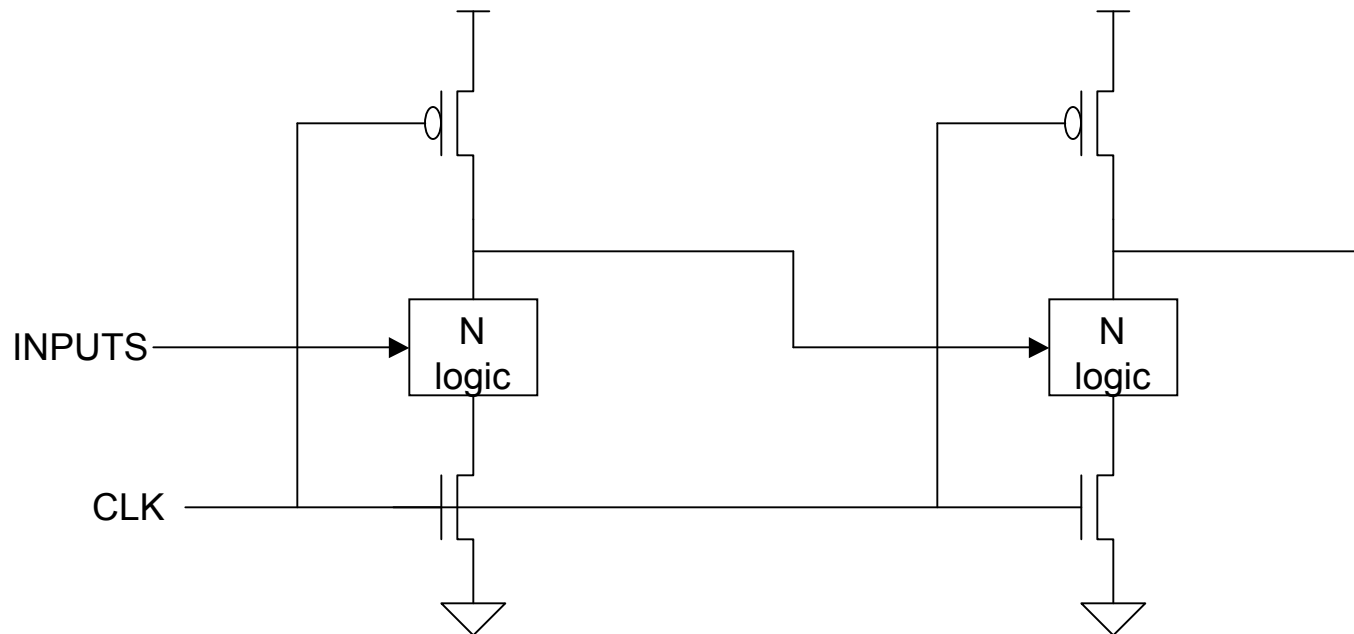

Since the evaluation from the first stage takes some time, the second stage will start evaluating with the precharged input rather than the evaluated input


# Cascading Dynamic Gates

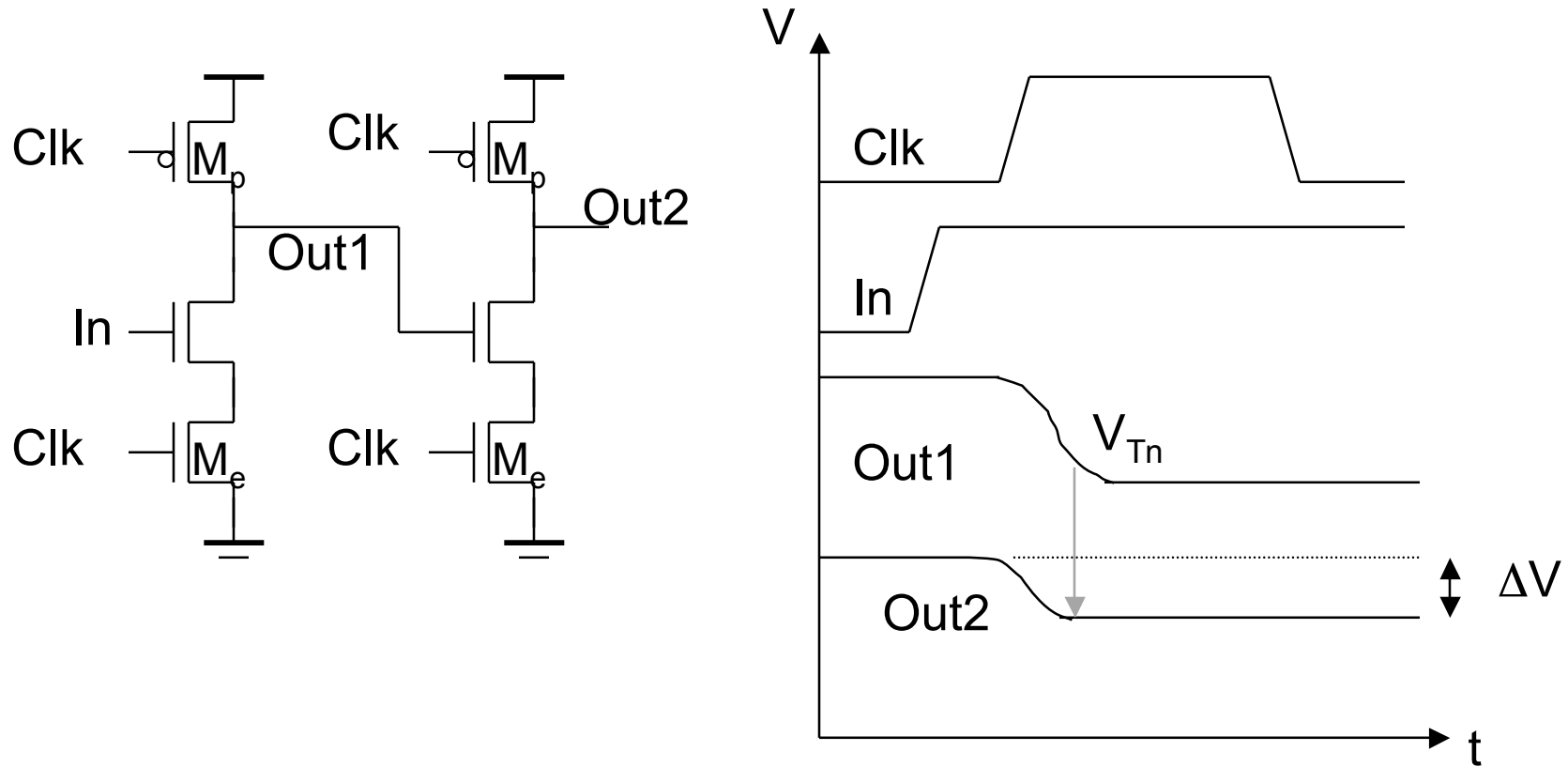

Only 0  $\rightarrow$  1 transitions allowed at inputs!

# Domino Logic


- Solves cascade problem

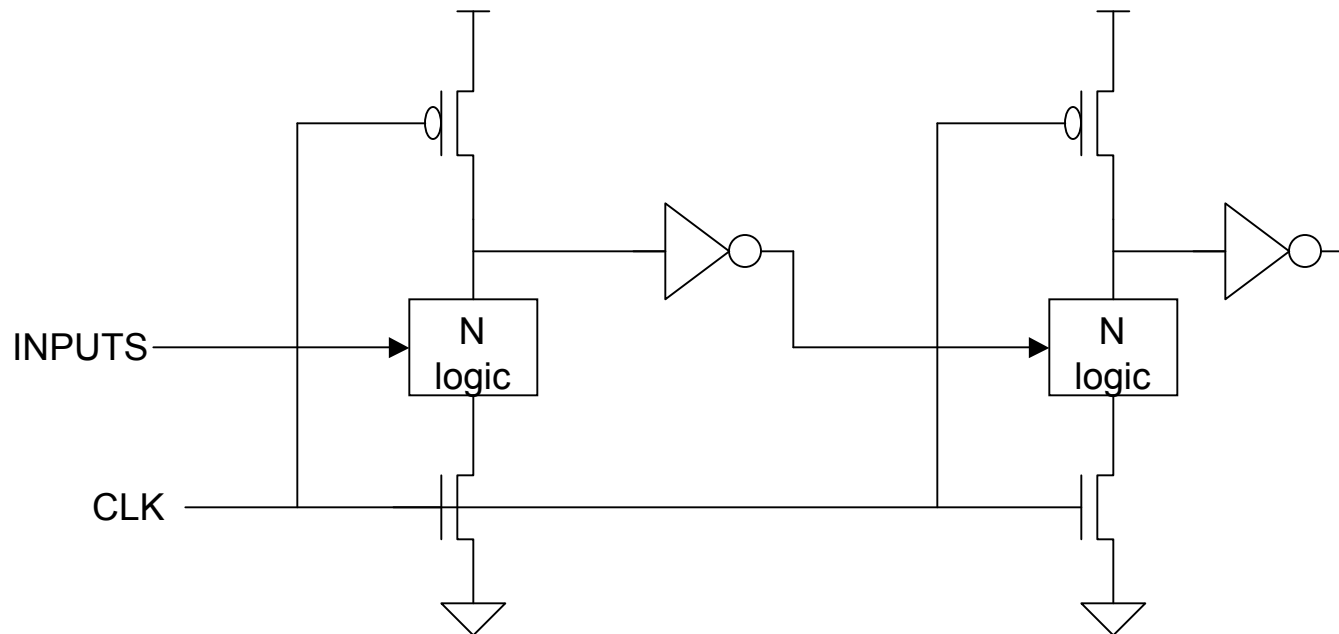

Since the precharged output from the first stage is 0, it will never activate the pulldown network in the second stage until the first stage evaluation has completed.



# NP Domino (Zipper) CMOS

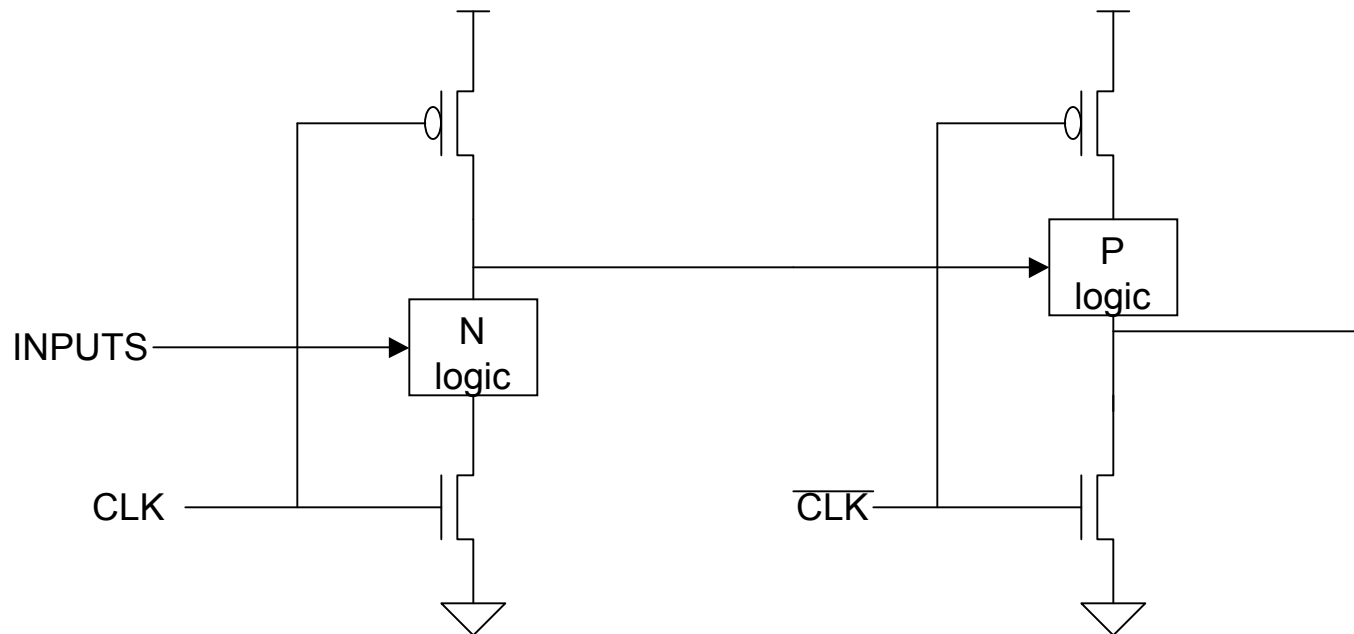

Since the second stage is build from p-logic, the precharged output from the first stage will not activate the inputs of the second stage



# Sequential Logic

- In our text:
  - a latch is level sensitive
  - a register is edge-triggered
  - a flip-flop is bistable
- There are many different naming conventions
  - For instance, many books call edge-triggered registers flip-flops as well

# Latch versus Register



## ❑ Latch

stores data when  
clock is low

  



## • Register

stores data when  
clock rises

 
 


# Latches

*Positive Latch*

  


*Negative Latch*

  


 
# Latch-Based Design

- N latch is transparent when  $\phi = 0$


- P latch is transparent when  $\phi = 1$




# Timing Definitions

 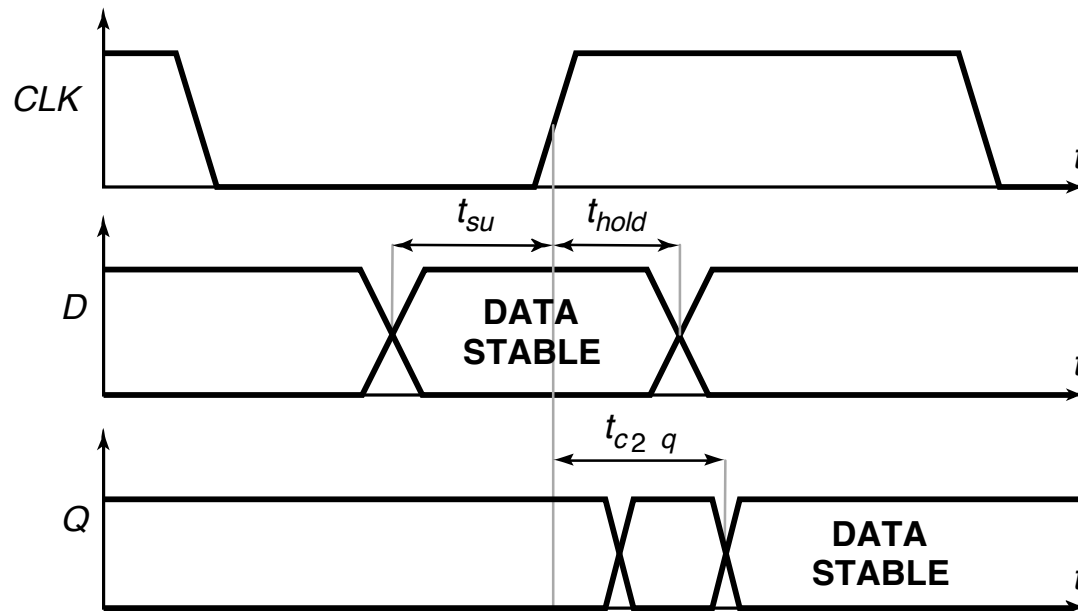

# Characterizing Timing

 


Register

 

Latch

# Maximum Clock Frequency

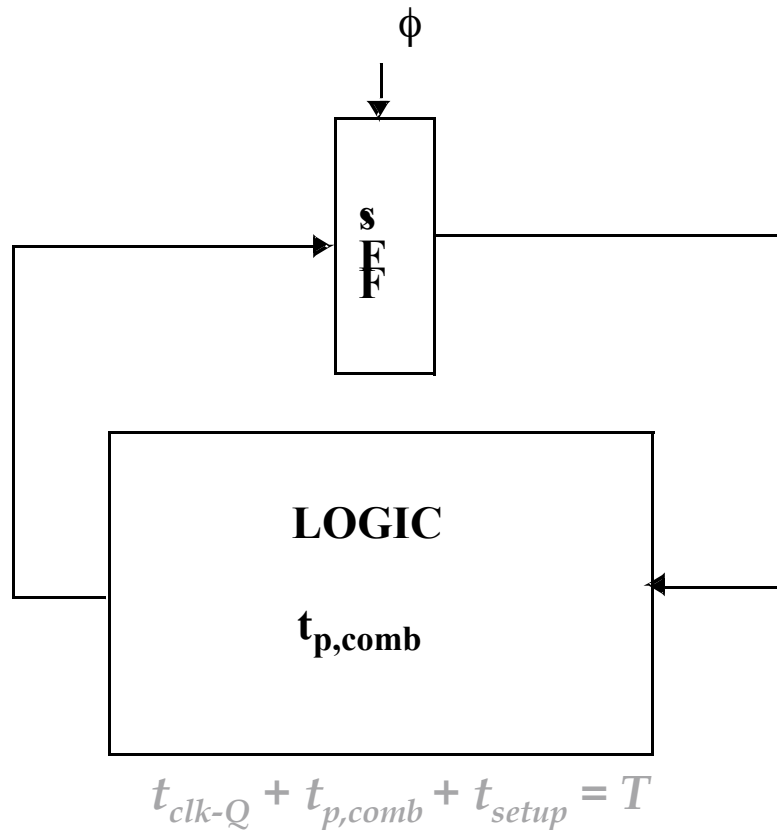


**Also:**

$$t_{cdreg} + t_{cdlogic} > t_{hold}$$



**$t_{cd}$ : contamination delay = minimum delay**



# Positive Feedback: Bi-Stability

 


# Meta-Stability

  


**Gain should be larger than 1 in the transition region**
 
# Writing into a Static Latch

Use the clock as a decoupling signal,  
that distinguishes between the transparent and opaque states



Converting into a MUX

 


Forcing the state  
(can implement as NMOS-only)

# Mux-Based Latches

Negative latch


(transparent when CLK= 0)

 

$$Q = \overline{Clk} \cdot Q + Clk \cdot In$$


Positive latch

(transparent when CLK= 1)

 


$$Q = Clk \cdot Q + \overline{Clk} \cdot In$$


# Mux-Based Latch

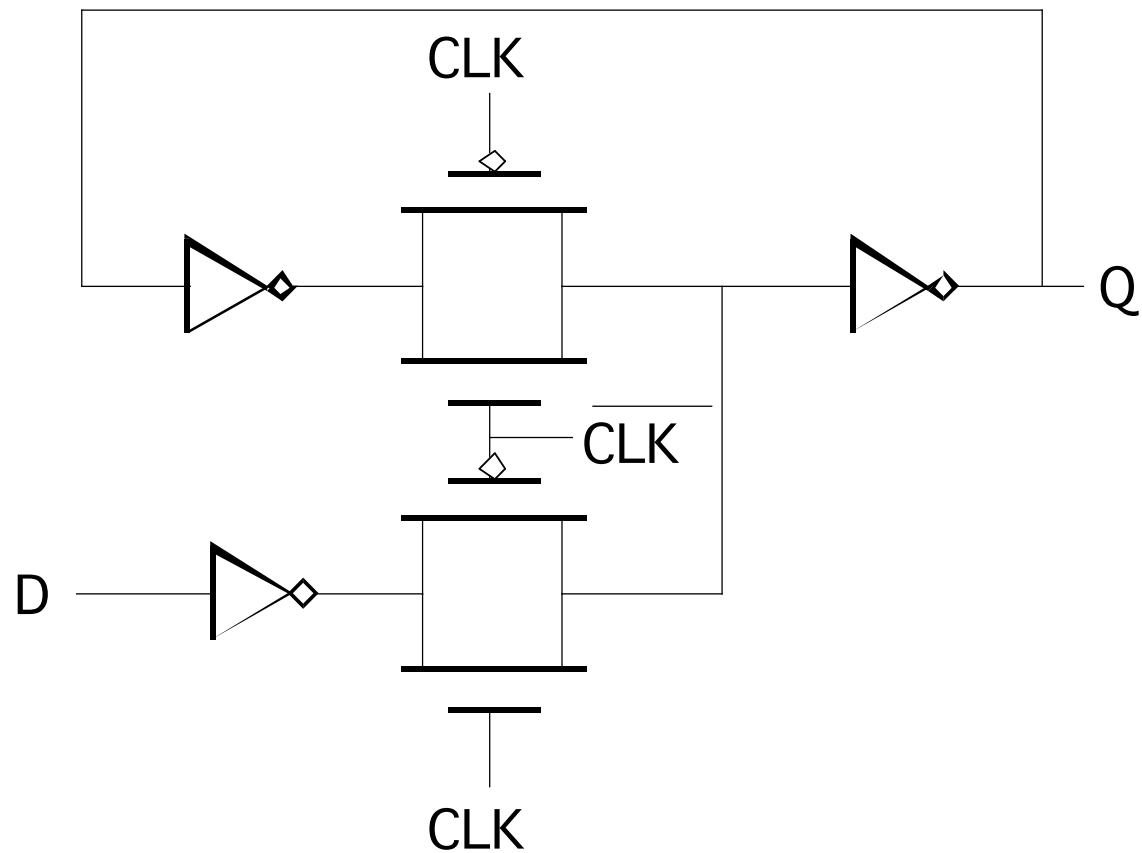

# Mux-Based Latch

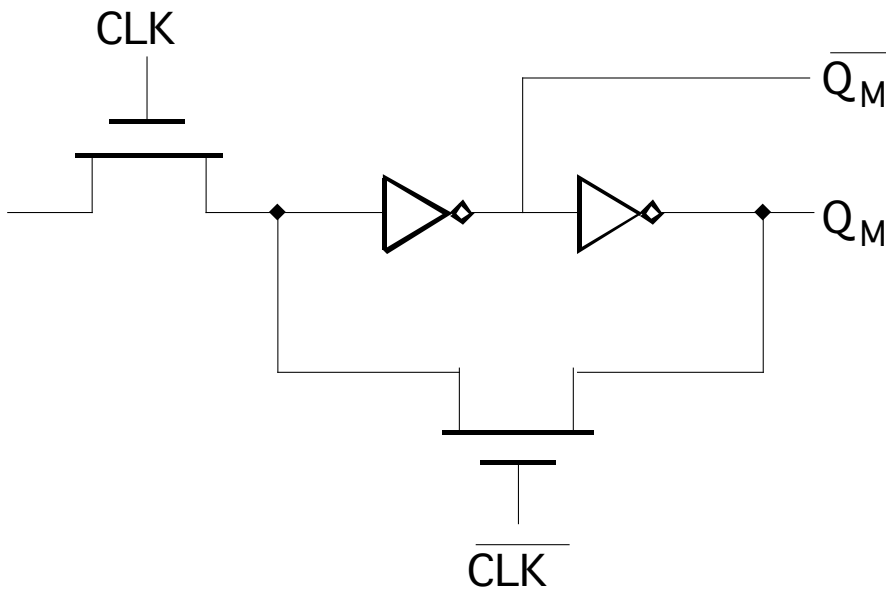


NMOS only

 

Non-overlapping clocks


# Master-Slave (Edge-Triggered) Register

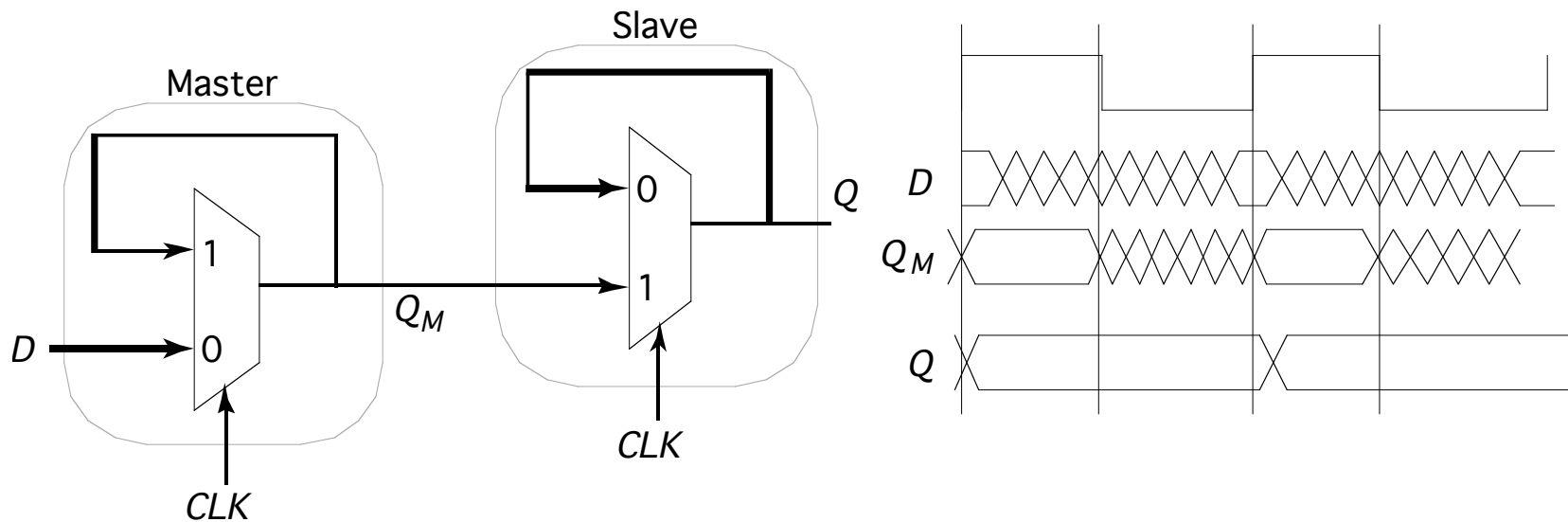

Two opposite latches trigger on edge  
Also called master-slave latch pair

# Master-Slave Register

## Multiplexer-based latch pair

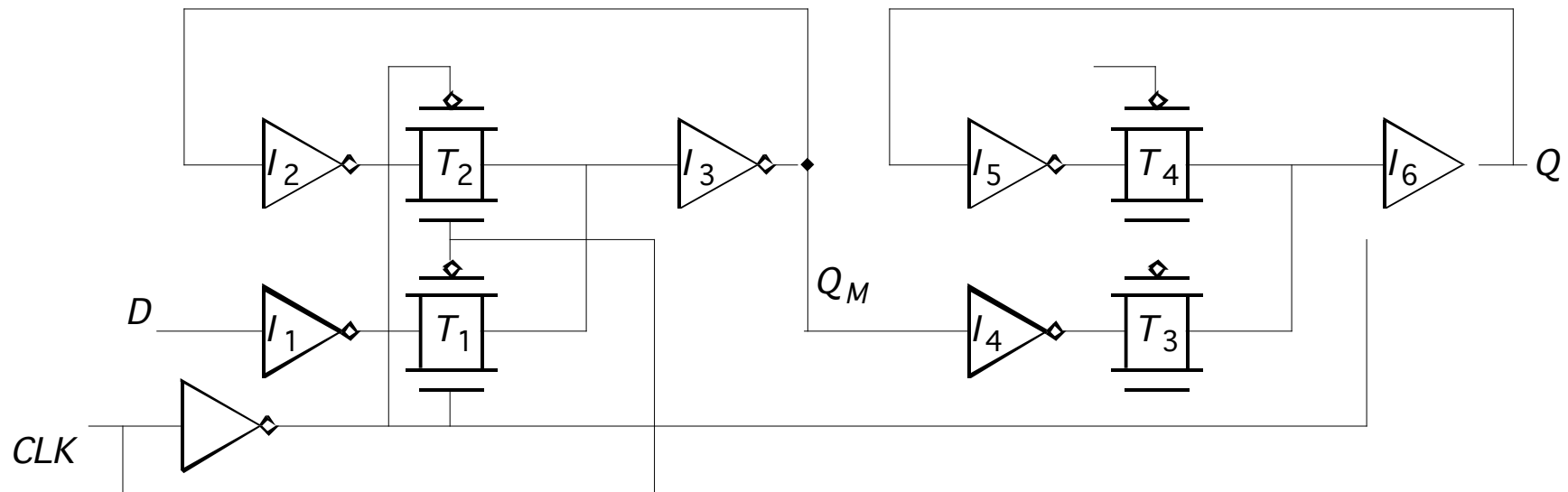




# Semiconductor Memory Classification

Read-Write Memory		Non-Volatile Read-Write Memory	Read-Only Memory
Random Access	Non-Random Access	EPROM E <sup>2</sup> PROM  FLASH	Mask-Programmed Programmable (PROM)
SRAM  DRAM	FIFO  LIFO Shift Register  CAM		


# Memory Design

- Random Access Memory

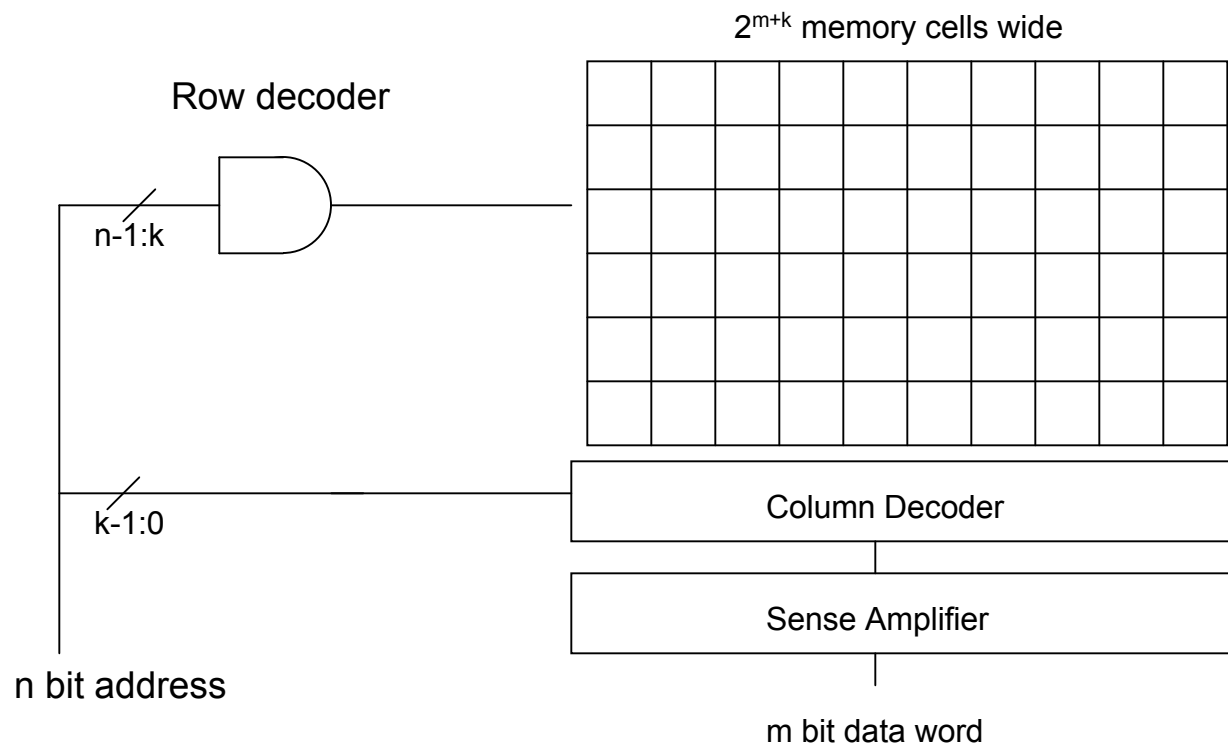

# Memory Design

- Static RAM Cell

 


# Memory Design


- Reads are straightforward
  - May need precharge circuitry to pull up bit line
- Writes are trickier
  - Use driver transistors that will pull-up or pull-down bit line as necessary

# Memory Design


- Static RAM Cell with precharge

 

- Static RAM Cell write circuitry

 

# 3-Transistor DRAM Cell

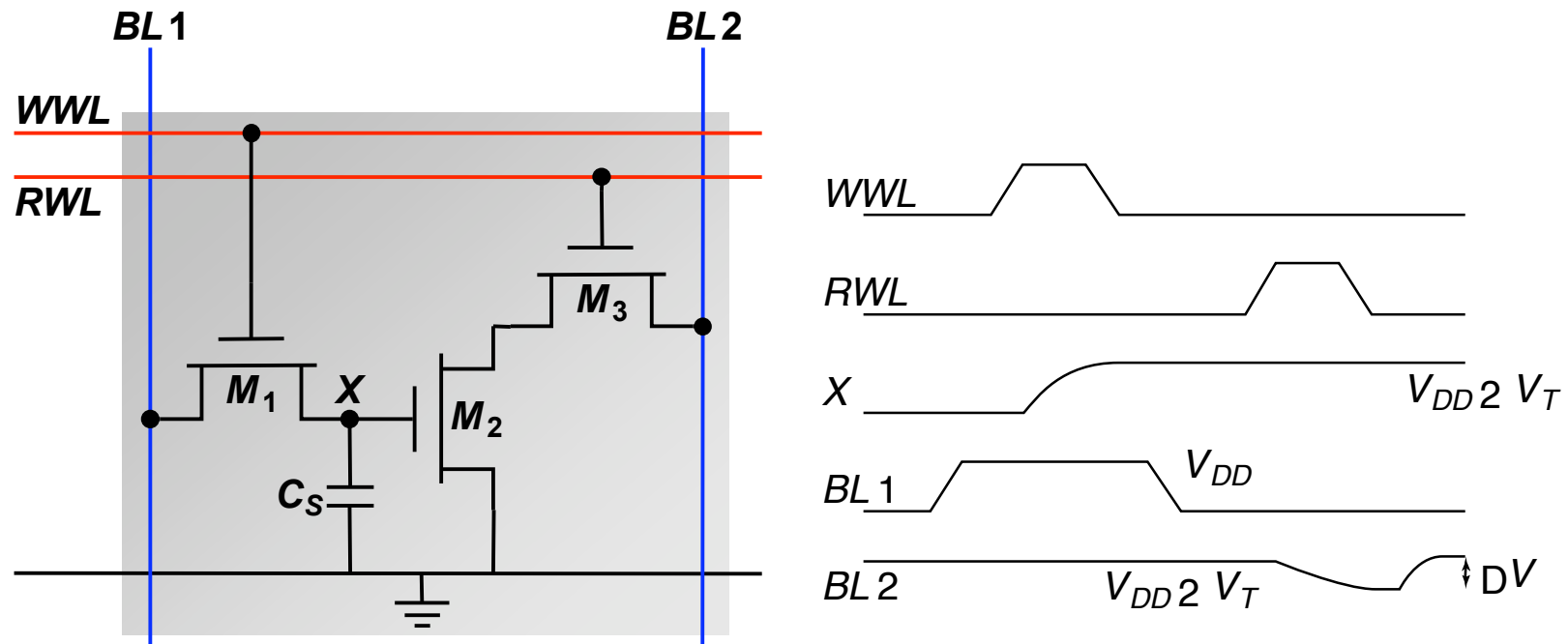


No constraints on device ratios

Reads are non-destructive



Value stored at node X when writing a “1” =  $V_{WWL} - V_{Tn}$

# 3T-DRAM — Layout

 



# 1-Transistor DRAM Cell

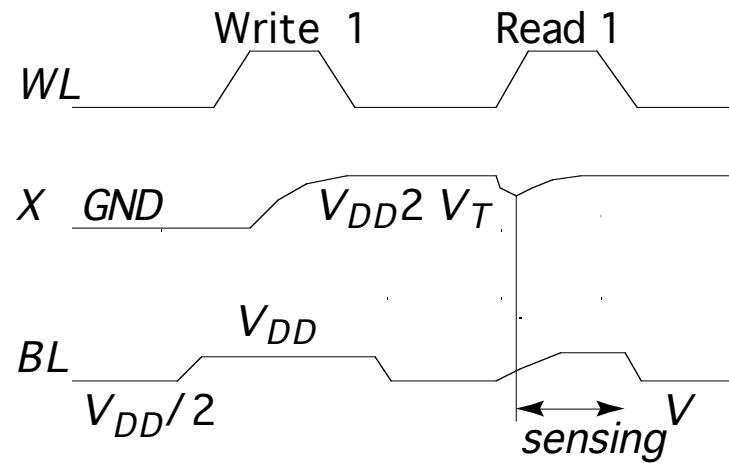 

**Write:**  $C_S$  is charged or discharged by asserting WL and BL.

**Read:** Charge redistribution takes places between bit line and storage capacitance


$$\Delta V = V_{BL} - V_{PRE} = V_{BIT} - V_{PRE} \frac{C_S}{C_S + C_{BL}}$$

**Voltage swing is small; typically around 250 mV.**


# DRAM Cell Observations

- ❑ 1T DRAM requires a sense amplifier for each bit line, due to charge redistribution read-out.
- ❑ DRAM memory cells are single ended in contrast to SRAM cells.
- ❑ The read-out of the 1T DRAM cell is destructive; read and refresh operations are necessary for correct operation.
- ❑ Unlike 3T cell, 1T cell requires presence of an extra capacitance that must be explicitly included in the design.
- ❑ When writing a “1” into a DRAM cell, a threshold voltage is lost. This charge loss can be circumvented by bootstrapping the word lines to a higher value than  $V_{DD}$


# Sense Amp Operation

 

# 1-T DRAM Cell

 

**Cross-section**

 

**Layout**

**Uses Polysilicon-Diffusion Capacitance**  
**Expensive in Area**

# Memory Design

- RAMs
  - Static RAM is faster, does not need to be refreshed
  - Dynamic RAM is more compact

# Next class

- More about memory
- Control logic